

Understanding basic electronics and resistance for Arduino

To understand how electronic circuits work and how to use them. There are some basic definitions you need to learn.

Sensors: These are components that convert other forms of energy into electrical energy that you can read. Switches, knobs, potentiometers, light, and motion sensors fall in this category.

Actuators: convert electrical energy into other forms such as light bulbs, motors, and LEDs are all actuators.

Electricity: this is the flow of electrical energy through conductive materials. An electrical circuit consists of two elements: a power source and components that transform electrical energy into other forms of energy.

Electronics: electronics refers to reading changes in electrical properties as information. For example, a microphone changes sound pressure waves in the air into changing electrical voltage. The process of changing energy into another is called **transduction**. Devices that enable this are called **transducers**.

To use transduction with Arduino, you must learn something about electricity. Therefore some definitions are given below to understand a few things about electricity. After that, we will look into some electrical properties and components and the relationship between some of the terms.

Voltage: is a measure of the difference in electrical potential energy between two points in a circuit. Voltage is measured in Volts.

Current: a measure of the magnitude of electrons flow through a particular point of the circuit. This point is measured in Amperes or Amps. Since the current we are using is low with Arduino Boards, we will code most of the time with MilliAmps (mA).

Resistance: is a measure of the material's ability to oppose the flow of electricity. Resistance is measured in ohms.

Resistors: resistors resist but do not block (totally) the flow of electricity. They are used to control the flow of current. Current can move either way through a resistor, so it doesn't matter which way you connect the resistor in a circuit. Their resistance measures resistors in ohms (Ω), often seen as kilohms (K Ω).

Resistance: Ohm's LAW


One important aspect of electronics is to make sure that you protect your electronic components from over current. The most common way to do that is by adding resistors. It is essential to understand the method to determine the resistor that is needed. Therefore, Ohm's it is wise to learn more about Ohm's Law.

Every circuit that we will make must have a source of electrical energy and a load that uses that energy. All of the electrical energy in a circuit has to be used by the load. The load will convert that energy into some other form of energy.

A circuit with no load is called a short circuit. In other words, the power source feeds all of its power through wires back to itself. Your Arduino board or components may melt or blow up.

Figure LED with battery – this circuit is not right!

The figure a very simple circuit consisting of a LED and a battery. The battery is the source, and the LED is the load. The electrical energy coming from the battery is converted to heat and light energy by the LED. All the energy is used in the process. However, the LED cannot take the voltage produced by the battery. (4.5V is supplied while the LED can handle 2V). How can we not overload the circuit? The answer is quite simple. We can use Ohm's Law to figure out what kind of resistance we need.

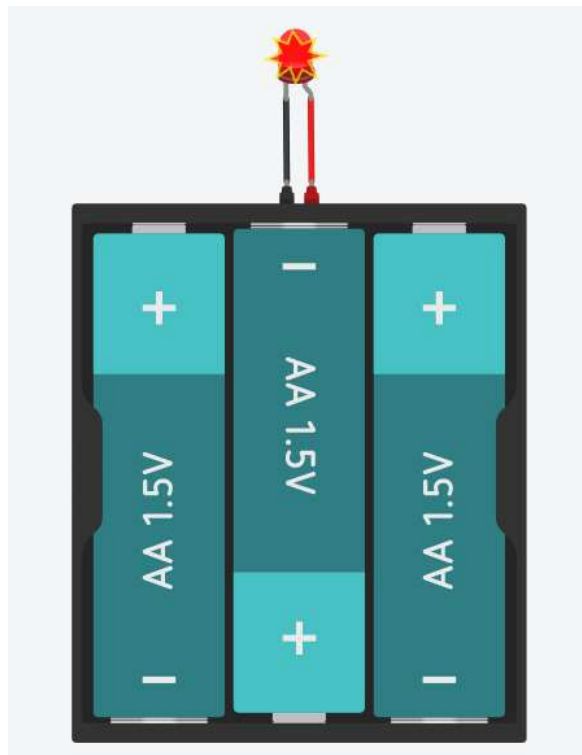

Ohm's Law : $V = I \times R$

V = Voltage

I = Current

R = Resistance

To get the V in the formula, we need to know two things. The voltage of the power supply and the voltage of the load (led).

Led with resistor

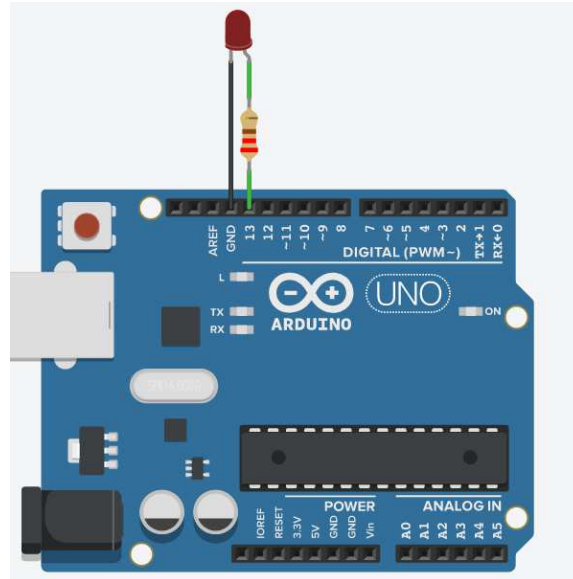


Figure 2. The correct way to connect a LED to an Arduino Uno Board with Resistor.

The Arduino Uno Board will provide 5v of power, and we are wiring a LED to the power source with a resistor. The Arduino board itself receives power from a USB connector or a dc power supply.

*In any loop of the circuit, the voltage must be balanced: the amount **voltage generated = the amount used.***

So what does this have to do with Forward Voltage? LEDs have a characteristic called “*forward voltage*,” which is on the datasheet as V_F . This forward voltage is the voltage “used” by the LED at a certain reference current. In the circuit above, 5V is one part of the loop, and the other half must use the 5V (to ensure the balance).

Whenever a LED is on, the voltage is used somewhere between 1.85V and 2.5V. So let’s assume 2.2V as an average. Standard red, orange, yellow, and yellow-green LEDs have V_f of about 1.8V, while pure-green, blue and white have a V_f of about 3.3V

Check the datasheet of your LED to make sure you choose the right voltage Forward

If we subtract the Forward Voltage(2.2V) from the power source (5V) we are left with 2.8V. This is the voltage that must be absorbed by the resistor to create the balance in the circuit.

$$5V \text{ (power source)} - 2.2V \text{ (LED forward voltage)} = 2.8V$$

The next part of the equation is to know the I , which is current, to drive the LED. LEDs have a maximum current (I_f or I_{max} on the datasheet). This is often around 25 – 30mA. Slightly under the maximum, we choose our value. Let’s say 20mA.

Note: You can always give an LED less current. Running the LED near its maximum gives you maximum brightness. If you choose to dim the LED, it will cost power dissipation (heat) and battery life (if you use a battery).

So we are choosing 20mA as the desired current for the LED. With this determined, we can pick a resistor.

$$2.8 \text{ (V)} = 20\text{mA(I)} \times R \text{ or rephrased } 2.8\text{(v)} / 20 \text{ mA(I)} = R$$

If you are using mA, convert to A by dividing by 1000.

$$2.8 / 0.020 \text{ A} = 140$$

When we solve this, number 140 is returned. This 140 Ω or 140 ohms. We end up with a resistor value of 140 ohms.

Resistors are usually available in values such as 10 Ω , 12 Ω , 15 Ω and multiplies (150 Ω , 1.5 K Ω , 15K Ω)

So if the resistor value that is calculated is not a common value, such as 140 Ω , we usually pick the next higher number. In our case, that will be 150 Ω .

The brightness of the LED is controlled by the current. So, to dim an LED, we need to reduce the current. Recall Ohm's Law:

$$\mathbf{V = I \times R}$$

$$\mathbf{\text{Resistor value} = (V_{\text{supply}} - V_F) / I_F}$$

$$\mathbf{\text{Resistor Value} = (\text{Power Supply} - \text{Forward Voltage}) / \text{Current}}$$

Thus we can deduce the brightness (current) by either decreasing the voltage or increasing the resistance.